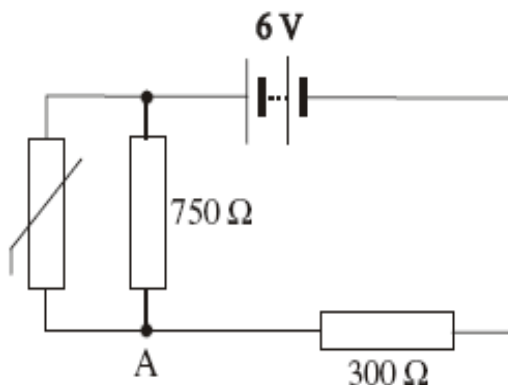


State Examination Commission – Physics Higher Level, 2005

Question 9

Define (i) potential difference, (ii) resistance. (12)

Two resistors, of resistance R_1 and R_2 respectively, are connected in parallel. Derive an expression for the effective resistance of the two resistors in terms of R_1 and R_2 . (12)



In the circuit diagram, the resistance of the thermistor at room temperature is 500Ω . At room temperature, calculate

(i) the total resistance of the circuit; (18)

(ii) the current flowing through the 750Ω resistor. (18)

As the temperature of the room increases, explain why

(iii) the resistance of the thermistor decreases; (14)

(iv) the potential at A increases. (14)

Define (i) potential difference, (ii) resistance. (6)

Standard definitions – Must know

Two resistors, of resistance R_1 and R_2 respectively, are connected in parallel. Derive an expression for the effective resistance of the two resistors in terms of R_1 and R_2 . (12)


In a parallel circuit, $I = I_1 + I_2$

The pd across each resistor in the circuit is the same, and is the same as the terminal pd of the battery, V_s .

Using Ohm's law, $V = IR$, and therefore, $I = V/R$.

$$\begin{aligned} \text{Since } I &= I_1 + I_2, \\ V/R &= V/R_1 + V/R_2 \end{aligned}$$

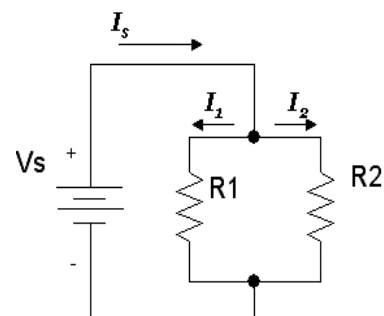Dividing through by V , $1/R = 1/R_1 + 1/R_2$



In the circuit diagram, the resistance of the thermistor at room temperature is 500Ω . At room temperature, calculate:

(i) the total resistance of the circuit. (9)

$$1/R_p = 1/500 + 1/750$$

$$R_p = 300 \Omega$$

$$R_T = 300 + 300 = 600 \Omega$$

(ii) the current flowing through the 750Ω resistor. (9)

$$I_T = (V/R)_T = 6 \div 600 = 0.01 \text{ A}$$

$$\text{P.d. across } 300 \Omega \text{ resistor} = (0.01)(300) = 3 \text{ V}$$

Therefore, pd across $750 \Omega = 6 - 3 = 3 \text{ V}$

So, Current through 750Ω Resistor = $V/R = 3 \div 750 = 4 \times 10^{-3} \text{ A} = 4 \text{ mA}$

As the temperature of the room increases, explain why (iii) the resistance of the thermistor decreases (7)

As the room temperature rises, more electrons are released into the conduction band and become available to carry charge (to conduct), i.e., the resistance drops.

(iv) the potential at A increases. (7)

Because the resistance of the thermistor drops, the resistance of the two resistors in parallel combination also drops which means the p.d. dropped across this combination is smaller and the potential at A increases.